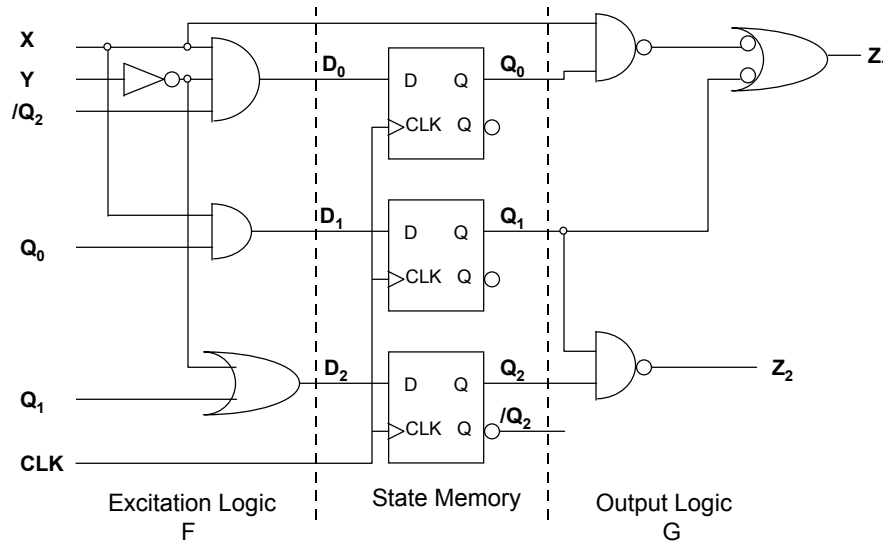


Example 2 - State Machine with D Flip-flops



Flaxer Eli - Logic Design

Ch 7b - 1

Example 2 - Equations

- Excitation Equations

$$D_0 = X Y' Q_2'$$

$$D_1 = X Q_0$$

$$D_2 = Y' + Q_1$$

- Characteristic Equation for D flip-flop

$$Q^* = D$$

- Next State or Transition Equations

$$Q_0^* = D_0 = X Y' Q_2'$$

$$Q_1^* = D_1 = X Q_0$$

$$Q_2^* = D_2 = Y' + Q_1$$

- Output Equations

$$Z_1 = X Q_0 + Q_1' \quad (\text{mealy})$$

$$/Z_2 = (Q_1 Q_2)' \quad (\text{moore})$$

Thus, this is a mealy machine

$$\begin{array}{c} X \ Y \ Q_2 \ Q_1 \ Q_0 \\ 1 \ 0 \ 0 \ - \ - \\ 1 \ - \ - \ 1 \\ - \ 0 \ - \ - \ \text{or} \ - \ - \ 1 \ - \end{array}$$

Flaxer Eli - Logic Design

Ch 7b - 2

Example 2 - Transition / Output table

state name	Q2	Q1	Q0	XY			
				00	01	11	10
A=	0	0	0	100, 11	000, 11	000, 11	101, 11
B=	0	0	1	100, 11	000, 11	010, 11	111, 11
C=	0	1	0	100, 01	100, 01	100, 01	101, 01
D=	0	1	1	100, 01	100, 01	110, 11	111, 11
E=	1	0	0	100, 11	000, 11	000, 11	100, 11
F=	1	0	1	100, 11	000, 11	010, 11	110, 11
G=	1	1	0	100, 00	100, 00	100, 00	100, 00
H=	1	1	1	100, 00	100, 00	110, 10	110, 10

Q2* Q1* Q0*, Z1 /Z2
(Next State, Outputs)

Transition Equations

$$Q0^* = D0 = X Y' Q2'$$

$$Q1^* = D1 = X Q0$$

$$Q2^* = D2 = Y' + Q1$$

Output Equations

$$Z1 = X Q0 + Q1'$$

$$/Z2 = (Q1 Q2)'$$

X Y Q2 Q1 Q0

$$1 0 0 - -$$

$$1 - - - 1$$


$$- 0 - - - \text{ or } - - - 1 -$$

Example 2 - State / Output table

S	XY			
	00	01	11	10
A	E, 11	A, 11	A, 11	F, 11
B	E, 11	A, 11	C, 11	H, 11
C	E, 01	E, 01	E, 01	F, 01
D	E, 01	E, 01	G, 11	H, 11
E	E, 11	A, 11	A, 11	E, 11
F	E, 11	A, 11	C, 11	G, 11
G	E, 00	E, 00	E, 00	E, 00
H	E, 00	E, 00	G, 10	G, 10

S*, Z1 /Z2

Example 2 - State Diagram

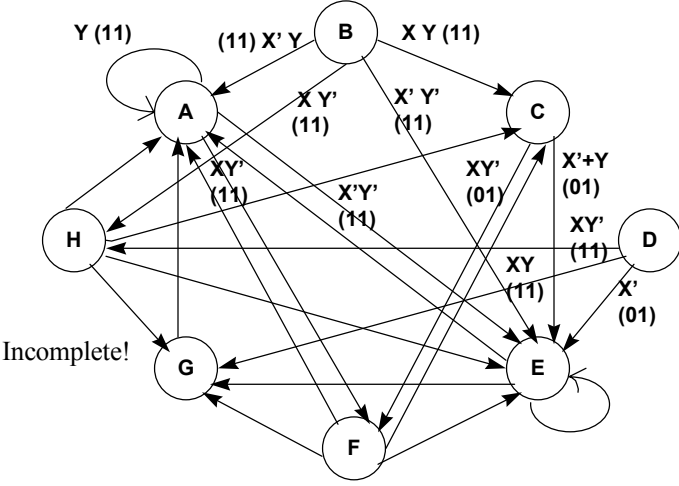

Incomplete!

Different format
Arc: input expression (outputs) = xy (Z1 /Z2)

