

Chapter 1


Combinational Logic

Process Control

Chapter Outline


- Documentation Standards for digital systems.
- Combinational Logic Design Structures :
 - Logic Gates
 - Decoders
 - Encoders
 - Three-State Buffers
 - Multiplexers
 - Demultiplexers
 - Adders

Basic logic Gates

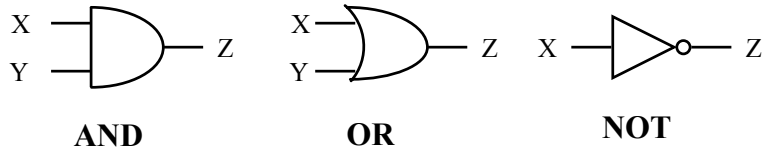


X	Y	Z		X	Y	Z		X	Z
0	0	0		0	0	0		0	1
0	1	0		0	1	1		1	0
1	0	0		1	0	1			
1	1	1		1	1	1			

No Basic logic Gates

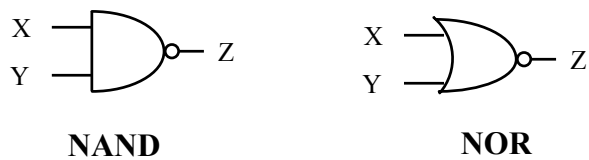


X	Y	Z				X	Y	Z
0	0	1				0	0	1
0	1	1				0	1	0
1	0	1				1	0	0
1	1	0				1	1	0

No Basic logic Gates

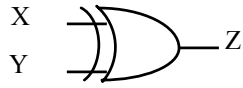


XOR

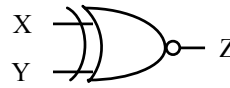



NXOR

X	Y	Z				X	Y	Z
0	0	0				0	0	1
0	1	1				0	1	0
1	0	1				1	0	0
1	1	0				1	1	1


Timing Diagrams

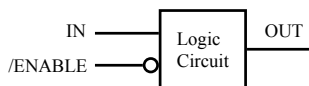

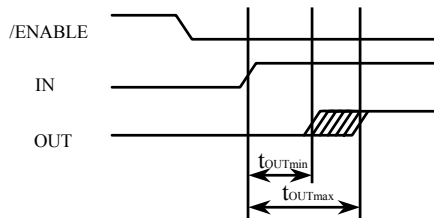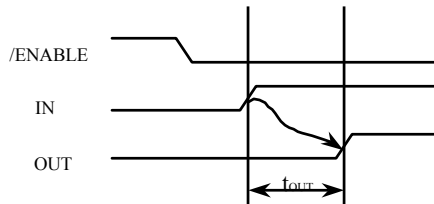- Delay depends on
 - Internal circuit structure
 - Logic Family type
 - Source Voltage
 - Temperature




Timing Diagram for Data signals (Bus)

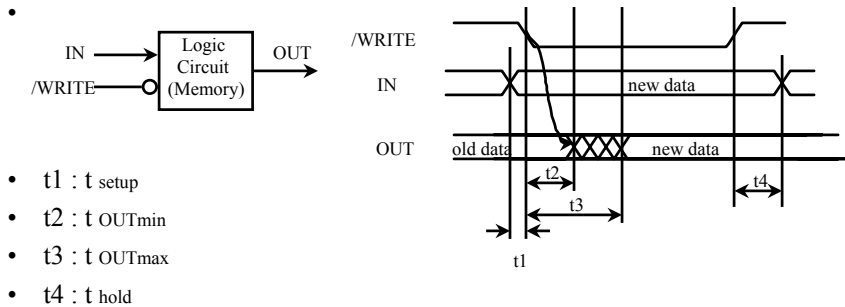

Decoder

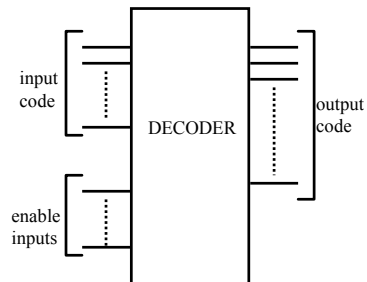
- Multiple-input/multiple-output device.
- Inputs (n) are less than outputs (m).
- Converts input code words into output code words.
- One-to-One mapping :
 - Each input code produces only one output code.
- Input codes :
 - Binary Code
 - Gray Code
 - BCD Code
 - Your Code !



Binary Decoder


- n-to- 2^n decoder : n inputs and 2^n outputs.
- Input code : Binary Code.
- Output code : 1-out-of- 2^n , One output is asserted for each input code.
- Example : n=2, 2-to-4 decoder
-

Inputs			Outputs			
EN	I ₁	I ₀	Y ₃	Y ₂	Y ₁	Y ₀
0	x	x	0	0	0	0
1	0	0	0	0	0	1
1	0	1	0	0	1	0
1	1	0	0	1	0	0
1	1	1	1	0	0	0

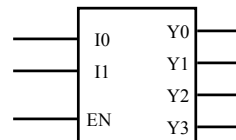

Encoders

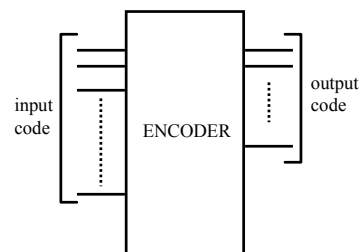
- Multiple-input/multiple-output device.
- Performs the inverse function of a Decoder.
- Outputs (m) are less than inputs (n).
- Converts input code words into output code words.



Binary Encoder

- 2^n -to- n encoder : 2^n inputs and n outputs.
- Input code : 1-out-of- 2^n .
- Output code : Binary Code
- Example : $n=3$, 8-to-3 encoder


		Inputs								Outputs		
		I0	I1	I2	I3	I4	I5	I6	I7	Y0	Y1	Y2
1	0	0	0	0	0	0	0	0	0	0	0	0
0	1	0	0	0	0	0	0	0	0	0	0	1
0	0	1	0	0	0	0	0	0	0	0	1	0
0	0	0	1	0	0	0	0	0	0	0	1	1
0	0	0	0	1	0	0	0	0	1	0	0	0
0	0	0	0	0	1	0	0	0	1	0	1	0
0	0	0	0	0	0	1	0	0	1	1	0	0
0	0	0	0	0	0	0	1	0	1	1	1	0
0	0	0	0	0	0	0	0	1	1	1	1	1

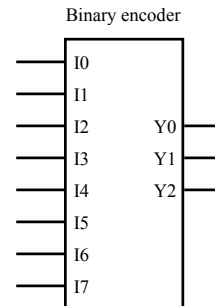

Priority Encoder

- 74x148


		Inputs								Outputs					
		/EI	/I0	/I1	/I2	/I3	/I4	/I5	/I6	/I7	/A2	/A1	/A0	/GS	/EO
1	x	x	x	x	x	x	x	x	x	x	1	1	1	1	1
0	x	x	x	x	x	x	x	x	0	0	0	0	0	1	
0	x	x	x	x	x	x	0	1	1	0	0	1	0	1	
0	x	x	x	x	0	1	1	1	1	0	1	1	0	1	
0	x	x	x	0	1	1	1	1	1	1	0	0	0	1	
0	x	x	0	1	1	1	1	1	1	1	0	1	0	1	
0	0	1	1	1	1	1	1	1	1	1	1	0	0	1	
0	0	1	1	1	1	1	1	1	1	1	1	1	0	1	
0	1	1	1	1	1	1	1	1	1	1	1	1	1	0	

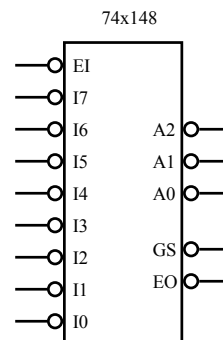

- /GS is asserted if any of the inputs is selected
- /EO is asserted when no input is selected (used for cascading encoders)

Three State Buffers/Drivers

- A buffer/inverter with enable input

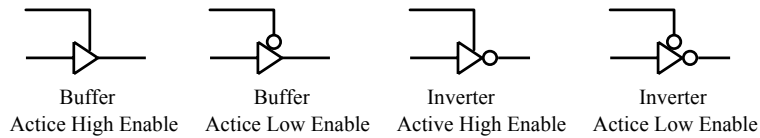


- The output is floating (High Impedance, Hi-Z) when the enable input is deasserted (The input is isolated from the output)
- Application:
Controlling the access of a single line/bus by multiple devices

Multiplexers

- Multiplexing : transmitting large number of signals over a small number of channels or lines
- Digital multiplexer (MUX) : selects one of many input lines and directs it to a single output.
- Selection lines controls the selection of a particular input
- n selection lines, 2^n inputs , single output.
- Example : 4-to-1 line multiplexer :
-


Function Table :

S1	S0	Y
0	0	I0
0	1	I1
1	0	I2
1	1	I3

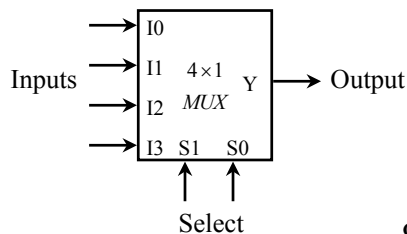

Demultiplexers

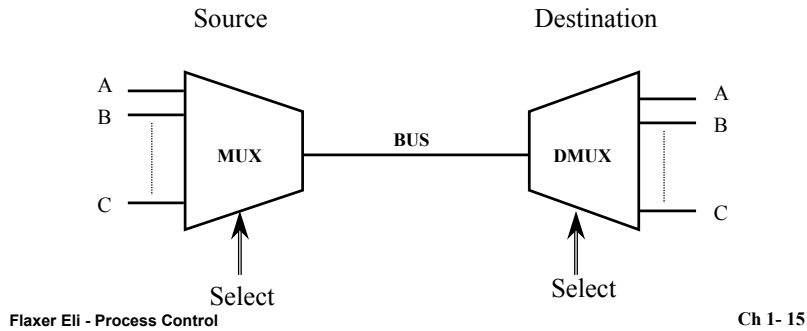- Demultiplexer (DMUX) performs the opposite function of a MUX.
- A digital Demultiplexer receives input data on a single input and transmits it on one of 2^n possible outputs according to the value of the n select inputs
- MUX/DMUX are used in data transmission




1-to-4 DMUX

- 1-to-4 DEMUX

Function Table


IN	S1	S0	D0	D1	D2	D3
x	0	0	IN	0	0	0
x	0	1	0	IN	0	0
x	1	0	0	0	IN	0
x	1	1	0	0	0	IN

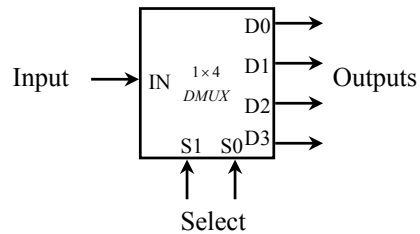

Half Adder

- Truth table :

X	Y	S=(X+Y)	CO
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

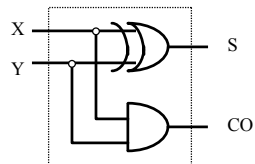


- $S = X \oplus Y$

$$CO = X \cdot Y$$

Full Adder

- Truth Table

X	Y	CIN	S	COUT
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

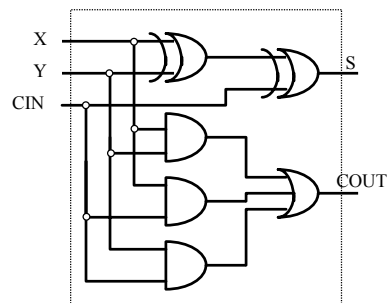

- $S = X'Y'CIN + X'YCIN' + XY'CIN' + XYCIN$

$$S = X \oplus Y \oplus CIN$$

- $COUT = XY + X CIN + Y CIN$

