

Chapter 2

Sequential Logic Design

Process Control


Logic Devices

- Logic devices divide into two major types:
- **Combinational Logic**
 - Current output depends on current input only
 - Gates, decoders, multiplexers, ALUs
- **Sequential Logic**
 - Current output depends on past inputs as well as current input
 - Thus has a memory (usually called the state)
 - Latches, flip-flops, state machines, counters, shift registers

Sequential Logic Definitions

- **Clock** - the master timing element behind the state changes of most sequential circuits.
 - a clock signal is active high if the state changes occur at the rising edge
 - and active low if state changes occur at the falling edge.
- **Clock Period** - time between successive transitions in the same direction.
- **Clock Frequency** - reciprocal of the clock period.
- **Duty Cycle** - the percentage of time that a clock is at its assertion level.

Clock Characteristics

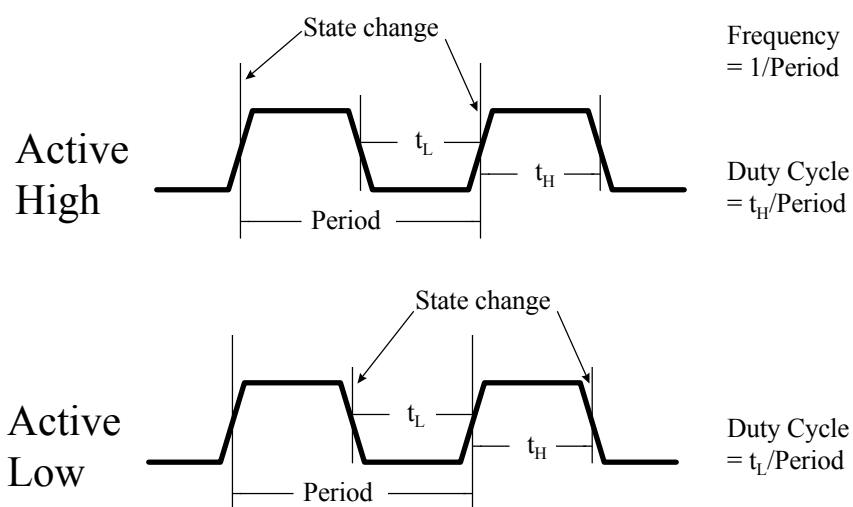

What Are Latches and Flip-flops?


- Common feedback sequential circuits
- Latch
 - Single-bit storage (memory)
 - Changes state at any time due to input change
- Flip-flop
 - Also single-bit storage
 - Changes state ONLY when a clock edge or pulse is applied

Types of Latches and Flip-flops

- Latches
 - S-R Latch
 - S-R Latch with Enable
 - D Latch
- Flip-flops
 - Edge-Triggered D Flip-Flop
 - Edge-Triggered S-R Flip-Flop
 - Edge-Triggered J-K Flip-Flop
 - T Flip-Flop

S-R Latch

Symbol

 


Hold
Reset
Set
ILLEGAL

Function Table

S	R	Q	/Q
0	0	Last Q	Last /Q
0	1	0	1
1	0	1	0
1	1	0	0


Schematic

 


Consider:

Timing Diagram
Propagation delay
Minimum pulse width
Oscillation


D Flip-Flop

 


C	D	Q	/Q
1	0	0	1
1	1	1	0
0	X	Last Q	Last /Q

 

 
Store a data bit, not set/reset
"Transparent latch"
No illegal operation problem
Setup and Hold time



Positive-Edge-Triggered D Flip-Flop

 


D	CLK	Q	/Q
0		0	1
1		1	0
X	0	Last Q	Last /Q
X	1	Last Q	Last /Q

 


D	CLK	Q	/Q
0		0	1
1		1	0
X	0	Last Q	Last /Q
X	1	Last Q	Last /Q

Negative-Edge-Triggered D Flip-Flop

 


D	CLK	Q	/Q
0		0	1
1		1	0
X	0	Last Q	Last /Q
X	1	Last Q	Last /Q

Edge-Triggered J-K Flip-Flop

 

J	K	C	Q	/Q
X	X	0	Last Q	Last /Q
X	X	1	Last Q	Last /Q
0	0	\uparrow	Last Q	Last /Q
0	1	\uparrow	0	1
1	0	\uparrow	1	0
1	1	\uparrow	Last /Q	Last Q


 


Flaxer Eli - Process Control

Ch 2 - 11


T (toggle) Flip-Flop

  - A T flip-flop changes state on every clock tick.
- Possible circuit designs
 - T without enable



T	CLK	Q	/Q
0	\uparrow	Q	/Q
1	\uparrow	/Q	Q
X	0	Q	/Q
X	1	Q	/Q

T with enable

 


Flaxer Eli - Process Control


Ch 2 - 12

Flip-Flop


D F.F.

 

SR F.F.

 

T F.F.

 

JK F.F.

